ExamGOAL
PYQ PDF

Free · With answer key

NEET · PHYSICS · CHAPTER-WISE PYQS

Alternating Current

NEET Physics · Previous Year Questions with Answer Key

65	34	2001 – 2026	English
QUESTIONS	PAPERS COVERED	YEARS	LANGUAGE

INSIDE THIS PDF

MCQ (Single Correct Answer)	64 questions
MCQ (More than One Correct Answer)	1 question
Answer key	at the end

Practise online

Every question with its full solution, free on **questions.examside.com**

1. **Solve**
   Print it, or work through it on screen.
2. **Check**
   The answer key is on the last pages.
3. **Understand**
   Scan the QR code beside any question for its full solution.

MCQ (Single Correct Answer) 64 questions

Q1. RE-NEET 2026

An ac voltage $V = 220 \sin\left(2 \times 10^3 t\right)$ Volt is applied to a series LCR circuit. Then the current amplitude in this circuit is:

(Given : $L = 10\text{mH}, C = 25\mu\,\text{F}, R = 100\Omega$)

(A) 22.0 A (B) 2.2 A (C) 5.5 A (D) 11.0 A

Open solution

Q2. NEET 2026

An ac circuit contains a resistance of $1\text{k}\Omega$, a capacitor of $0.1\mu\,\text{F}$ and an inductor of 1 mH connected in series. The resonance frequency of the circuit is approximately:

(A) 13.5 kHz (B) 10.1 kHz (C) 20.7 kHz (D) 15.9 kHz

Open solution

Q3. NEET 2026

The peak value of an alternating current is 5 A and frequency is 60 Hz . How long will the current, starting from zero, take to reach the peak value?

(A) $\frac{1}{120}$ s (B) $\frac{1}{60}$ s (C) $\frac{1}{30}$ s (D) $\frac{1}{240}$ s

Open solution

Q4. NEET 2025

To an ac power supply of 220 V at 50 Hz , a resistor of 20Ω, a capacitor of reactance 25Ω and an inductor of reactance 45Ω are connected in series. The corresponding current in the circuit and the phase angle between the current and the voltage is, respectively


(A) 15.6 A and 30° (B) 15.6 A and 45° (C) 7.8 A and 30° (D) 7.8 A and 45°

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

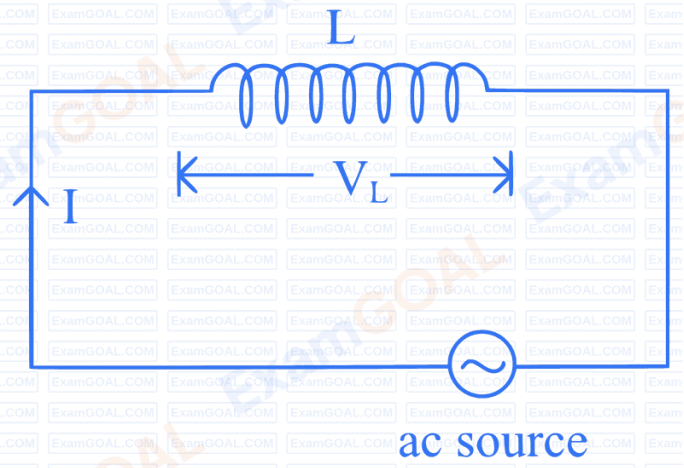Q5. NEET 2024 (Re-Examination)

In the circuit shown below, the inductance L is connected to an ac source. The current flowing in the circuit is $I = I_0 \sin \omega t$. The voltage drop (V_L) across L is



Open solution

(A) $\omega L I_0 \sin \omega t$
(B) $\frac{I_0}{\omega L} \sin \omega t$
(C) $\frac{I_0}{\omega L} \cos \omega t$
(D) $\omega L I_0 \cos \omega t$

Q6. NEET 2024 (Re-Examination)

A step up transformer is connected to an ac mains supply of 220 V to operate at 11000 V, 88 watt. The current in the secondary circuit, ignoring the power loss in the transformer, is

(A) 8 mA
(B) 4 mA
(C) 0.4 A
(D) 4 A

Open solution

Q7. NEET 2024 (Re-Examination)

The amplitude of the charge oscillating in a circuit decreases exponentially as $Q = Q_0 e^{-Rt/2L}$, where Q_0 is the charge at $t = 0$ s. The time at which charge amplitude decreases to $0.50Q_0$ is nearly:

[Given that $R = 1.5\Omega, L = 12$ mH, $\ln(2) = 0.693$]

(A) 19.01 ms
(B) 11.09 ms
(C) 19.01 s
(D) 11.09 s

Open solution

Q8. NEET 2024

In an ideal transformer, the turns ratio is $\frac{N_P}{N_S} = \frac{1}{2}$. The ratio $V_S : V_P$ is equal to (the symbols carry their usual meaning) :


(A) $1:2$
(B) $2:1$
(C) $1:1$
(D) $1:4$

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

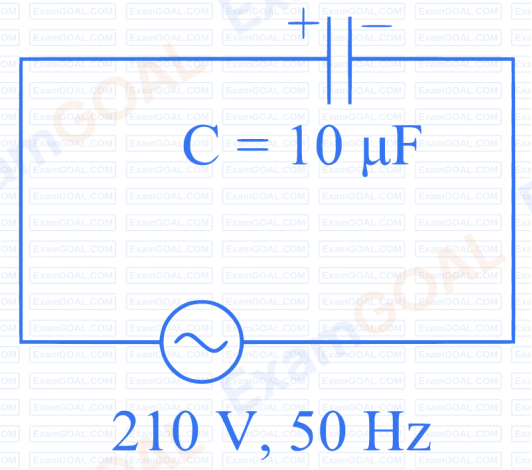Q9. NEET 2024

A $10\mu F$ capacitor is connected to a $210\ V, 50\ Hz$ source as shown in figure. The peak current in the circuit is nearly $(\pi = 3.14)$:




Open solution

(A) 0.58 A (B) 0.93 A (C) 1.20 A (D) 0.35 A

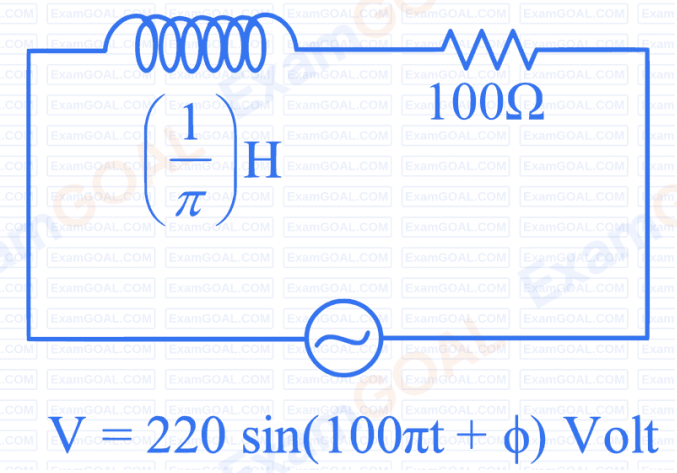Q10. NEET 2023 Manipur

An ac source is connected in the given circuit. The value of ϕ will be :




Open solution

(A) 60° (B) 90° (C) 30° (D) 45°

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

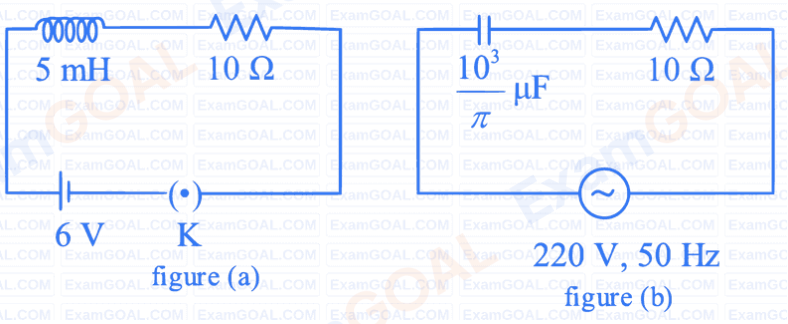Q11. NEET 2023 Manipur

If Z_1 and Z_2 are the impedances of the given circuits (a) and (b) as shown in figures, then choose the correct option



(A) $Z_1 < Z_2$ (B) $Z_1 + Z_2 = 20\ \Omega$ (C) $Z_1 = Z_2$ (D) $Z_1 > Z_2$

Open solution

Q12. NEET 2023 Manipur

The maximum power is dissipated for an ac in a/an:


(A) resistive circuit (B) LC circuit

(C) inductive circuit (D) capacitive circuit

Open solution

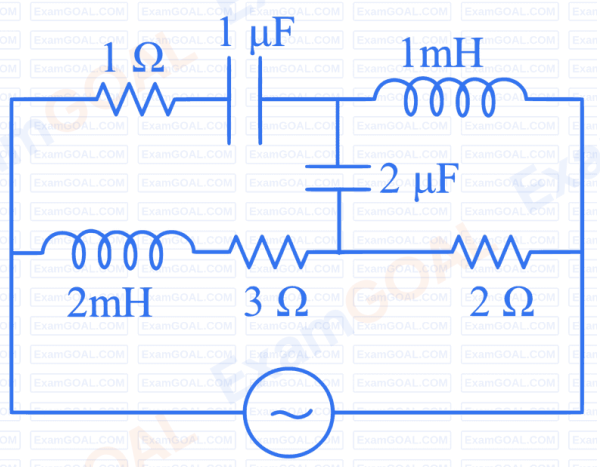Q13. NEET 2023 Manipur

For very high frequencies, the effective impedance of the circuit (shown in the figure) will be:-



(A) 4 Ω (B) 6 Ω (C) 1 Ω (D) 3 Ω

Open solution

Q14. NEET 2023

In a series LCR circuit, the inductance L is $10\ \text{mH}$, capacitance C is $1\ \mu\text{F}$ and resistance R is $100\ \Omega$. The frequency at which resonance occurs is :-

(A) 15.9 kHz (B) 1.59 rad/s (C) 1.59 kHz (D) 15.9 rad/s

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q15. NEET 2023

A $12\ \text{V}, 60\ \text{W}$ lamp is connected to the secondary of a step down transformer, whose primary is connected to ac mains of $220\ \text{V}$. Assuming the transformer to be ideal, what is the current in the primary winding ?

Open solution

(A) 2.7 A (B) 3.7 A (C) 0.37 A (D) 0.27 A

Q16. NEET 2023

An ac source is connected to a capacitor C. Due to decrease in its operating frequency

Open solution

(A) displacement current increases. (B) displacement current decreases.

(C) capacitive reactance remains constant. (D) capacitive reactance decreases.

Q17. NEET 2023

The magnetic energy stored in an inductor of inductance $4\ \mu\text{H}$ carrying a current of $2\ \text{A}$ is :


Open solution

(A) $4\ \text{mJ}$ (B) $8\ \text{mJ}$ (C) $8\ \mu\text{J}$ (D) $4\ \mu\text{J}$

Q18. NEET 2023

The net impedance of circuit (as shown in figure) will be :

Open solution

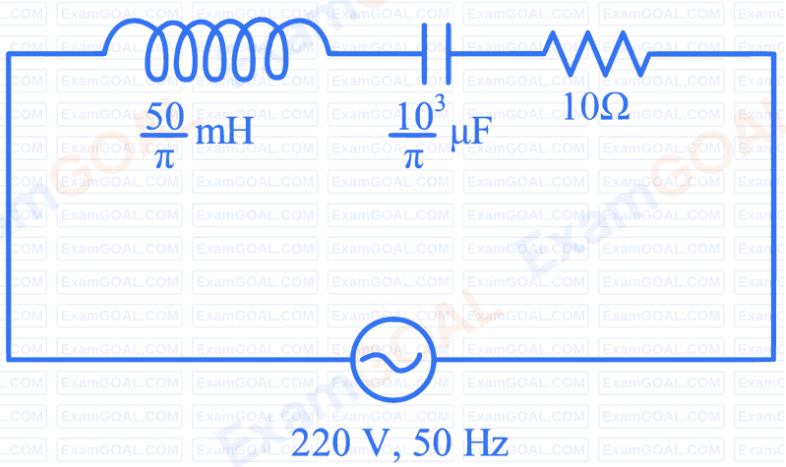

(A) 15Ω (B) $5\sqrt{5}\Omega$ (C) 25Ω (D) $10\sqrt{2}\Omega$

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q19. NEET 2022 Phase 2

Open solution

Given below are two statements

Statement I : In an a.c circuit, the current through a capacitor leads the voltage across it.

Statement II : In a.c circuit containing pure capacitance only, the phase difference between the current and voltage is π.

In the light of the above statements, choose the most appropriate answer from the options given below

(A) Statement I is incorrect but Statement II is correct

(B) Both Statement I and Statement II are correct

(C) Both Statement I and Statement II are incorrect

(D) Statement I is correct but Statement II is incorrect

Q20. NEET 2022 Phase 2

Open solution

An inductor of inductance 2 mH is connected to a 220 V, 50 Hz ac source. Let the inductive reactance in the circuit is X_1. If a 220 V dc source replace the ac source in the circuit, then the inductive reactance in the circuit is X_2. X_1 and X_2 respectively are :

(A) 0.628 Ω, infinity

(B) 6.28 Ω, zero

(C) 6.28 Ω, infinity

(D) 0.628 Ω, zero

Q21. NEET 2022 Phase 2

Open solution

A standard filament lamp consumes 100 W when connected to 200 V ac mains supply. The peak current through the bulb will be :

(A) 2 A

(B) 0.707 A

(C) 1 A

(D) 1.414 A

Q22. NEET 2022 Phase 1

Open solution

The peak voltage of the ac source is equal to

(A) The value of voltage supplied to the circuit

(B) The rms value of the ac source

(C) $\sqrt{2}$ times the rms value of the ac source

(D) $1/\sqrt{2}$ times the rms value of the ac source

Q23. NEET 2022 Phase 1

Open solution

A series LCR circuit with inductance 10 H, capacitance 10 μF, resistance 50 Ω is connected to an ac source of voltage, V = 200sin(100t) volt. If the resonant frequency of the LCR circuit is v_0 and the frequency of the ac source is v, then

(A) $v_0 = v = 50$ Hz

(B) $v_0 = v = \frac{50}{\pi}$ Hz

(C) $v_0 = \frac{50}{\pi}$ Hz, $v = 50$ Hz


(D) $v = 100$ Hz, $v_0 = \frac{100}{\pi}$ Hz

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q24. NEET 2021

An inductor of inductance L, a capacitor of capacitance C and a resistor of resistance 'R' are connected in series to an ac source of potential difference 'V' volts as shown in figure. Potential difference across L, C and R is 40V, 10V and 40V, respectively. The amplitude of current flowing through LCR series circuit is $10\sqrt{2}$ A. The impedance of the circuit is :

Open solution

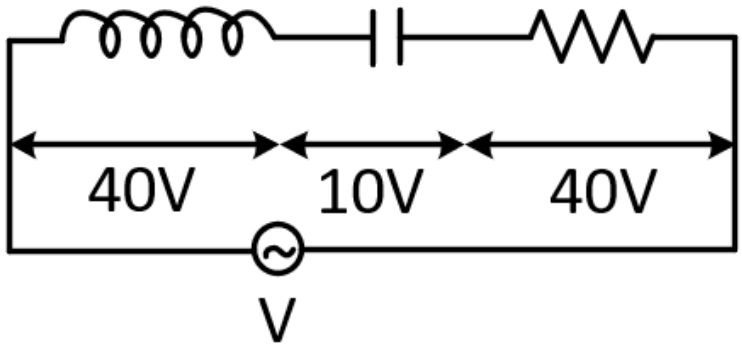

(A) 5Ω (B) $4\sqrt{2}\,\Omega$ (C) $5/\sqrt{2}\,\Omega$ (D) 4Ω

Q25. NEET 2021

A capacitor of capacitance 'C', is connected across an ac source of voltage V, given by

$V = V_0 \sin\omega t$

Open solution

The displacement current between the plates of the capacitor, would then be given by :

(A) $I_d = V_0\omega C \sin\omega t$ (B) $I_d = V_0\omega C \cos\omega t$

(C) $I_d = \frac{V_0}{\omega C}\cos\omega t$ (D) $I_d = \frac{V_0}{\omega C}\sin\omega t$

Q26. NEET 2021

A step down transformer connected to an ac mains supply of 220 V is made to operate at 11 V, 44W lamp. Ignoring power losses in the transformer, what is the current in the primary circuit ?

Open solution

(A) 4A (B) 0.2A (C) 0.4A (D) 2A

Q27. NEET 2021

A series LCR circuit containing 5.0 H inductor, 80μF capacitor and 40Ω resistor is connected to 230V variable frequency ac source. The angular frequencies of the source at which power transferred to the circuit is half the power at the resonant angular frequency are likely to be :

Open solution

(A) 42 rad/s and 58 rad/s (B) 25 rad/s and 75 rad/s

(C) 50 rad/s and 25 rad/s (D) 46 rad/s and 54 rad/s

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q28. NEET 2020 Phase 1

A 40 μF capacitor is connected to a 200 V, 50 Hz ac supply. The rms value of the current in the circuit is, nearly :

(A) 2.05 A (B) 2.5 A (C) 25.1 A (D) 1.7 A

Open solution

Q29. NEET 2020 Phase 1

A series LCR circuit is connected to an ac voltage source. When L is removed from the circuit, the phase difference between current and voltage is $\frac{\pi}{3}$. If instead C is removed from the circuit, the phase difference is again $\frac{\pi}{3}$ between current and voltage. The power factor of the circuit is :

(A) 0.5 (B) 1.0 (C) $-$ 1.0 (D) zero

Open solution

Q30. NEET 2018

The magnetic potential energy stored in a certain inductor is 25 mJ, when the current in the inductor is 60 mA. This inductor is of inductance

(A) 0.138 H (B) 138.88 H (C) 1.389 H (D) 13.89 H

Open solution

Q31. NEET 2018


An inductor 20 mH, a capacitor 100 μF and a resistor 50 Ω are connected in series across a source of emf, V = 10 sin 314 t. The power loss in the circuit is

(A) 0.79 W (B) 0.43 W (C) 2.74 W (D) 1.13 W

Open solution

Q32. NEET 2017

Figure shows a circuit that contains three identical resistors with resistance R = 9.0 Ω each, two identical inductors with inductance L = 2.0 mH each, and an ideal battery with emf $\varepsilon = 18V$. The current i through the battery just after the switch is closed is

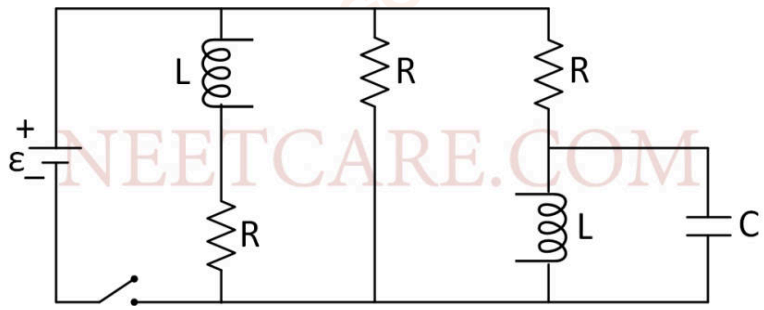

NEETCARE.COM

(A) 0.2 A (B) 4 A (C) 0 ampere (D) 2 mA

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q33. NEET 2016 Phase 2

Which of the following combinations should be selected for better tuning of an L-C-R circuit used for combination ?

Open solution

(A) R = 20 Ω, L = 1.5 H, C = 35 μF
(B) R = 25 Ω, L = 2.5 H, C = 45 μF
(C) R = 15 Ω, L = 3.5 H, C = 30 μF
(D) R = 25 Ω, L = 1.5 H, C = 45 μF

Q34. NEET 2016 Phase 2

The potential differences across the resistance, capacitance and inductance are 80 V, 40 V and 100 V respectively in an L-C-R circuit. The power factor of this circuit is

Open solution

(A) 0.4 (B) 0.5 (C) 0.8 (D) 1.0

Q35. NEET 2016 Phase 2

A 100 Ω resistance and a capacitor of 100 Ω reactance are connected in series across a 220 V source. When the capacitor is 50% charged, the peak value of the displacement current is

Open solution

(A) 2.2 A (B) 11 A (C) 4.4 A (D) $11\sqrt{2}A$

Q36. NEET 2016 Phase 1

An inductor 20 mH, a capacitor 50 μF and a resistor 40 Ω are connected in series across a source of emf V = 10 sin 340t. The power loss in A.C. circuit is

Open solution

(A) 0.76 W (B) 0.89 W (C) 0.51 W (D) 0.67 W

Q37. NEET 2016 Phase 1

A small signal voltage V(t) = V_0 sinωt is applied across an ideal capacitor C

Open solution

(A) Current $I(t)$ is in phase with voltage $V(t)$.
(B) Current $I(t)$ leads voltage V(t) by 180°
(C) Current $I(t)$, lags voltage $V(t)$ by 90°.
(D) Over a full cycle the capacitor C does not consume any energy from the voltage source.

Q38. AIPMT 2015

A series R-C circuit is connected to an alternating voltage source. Consider two situations :
(a) When capacitor is air filled.
(b) When capacitor is mica filled.
Current through resistor is I and voltage across capacitor is V then

Open solution

(A) $i_a > i_b$ (B) $V_a = V_b$ (C) $V_a < V_b$ (D) $V_a > V_b$

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q39. AIPMT 2015 Cancelled Paper

A resistance 'R' draws power 'P' when connected to an AC source. If an inductance is now placed in series with the resistance, such that the impedance of the circuit becomes 'Z'. the power drawn will be

Open solution

(A) $P\left(\frac{R}{Z}\right)$
(B) P
(C) $P\left(\frac{R}{Z}\right)^2$
(D) $P\sqrt{\frac{R}{Z}}$

Q40. AIPMT 2014

A transformer having efficiency of 90% is working on 200 V and 3 kW power supply. If the current in the secondary coil is 6 A, the voltage across the secondary coil and the current in the primary coil respectively are

Open solution

(A) 300 V, 15 A
(B) 450 V, 15 A
(C) 450 V, 13.5 A
(D) 600 V, 15 A

Q41. NEET 2013 (Karnataka)

The primary of a transformer when connected to a dc battery of 10 Volt draws a current of 1 mA. The number of turns of the primary and secondary windings are 50 and 100 respectively. The voltage in the secondary and the current drawn by the circuit in the secondary are respectively

Open solution

(A) 20 V and 2.0 mA
(B) 10 V and 0.5 mA
(C) Zero volt and therefore no current
(D) 20 V and 0.5 mA

Q42. NEET 2013

A coil of self-inductance L is connected in series with a bulb B and an AC source. Brightness of the bulb decreases when

Open solution

(A) a capacitance of reactance $X_C = X_L$ is included in the same citcuit.
(B) an iron rod is inserted in the coil.
(C) frequency of the AC source is decreased.
(D) number of turns in the coil is reduced.

Q43. AIPMT 2012 Mains

The instantaneous values of alternating current and voltage in a circuit are given as

Open solution

$i = \frac{1}{\sqrt{2}}$ sin (100 πt) ampere

$e = \frac{1}{\sqrt{2}} \sin\left(100\pi t + \frac{\pi}{3}\right)$ Volt

The average power in watts consumed in the circuit is

(A) $\frac{1}{4}$
(B) $\frac{\sqrt{3}}{4}$
(C) $\frac{1}{2}$
(D) $\frac{1}{8}$

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q44. AIPMT 2012 Prelims

Open solution

In an electrical circuit R, L, C and a.c. voltage source are all connected in series. When L is removed from the circuit, the phase difference between the voltage and the current in the circuit is $\frac{\pi}{3}$. If instead, C is removed from the circuit, the phase difference is again $\frac{\pi}{3}$. The power factor of the circuit is


(A) $\frac{1}{2}$ (B) $\frac{1}{\sqrt{2}}$ (C) 1 (D) $\frac{\sqrt{3}}{2}$

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

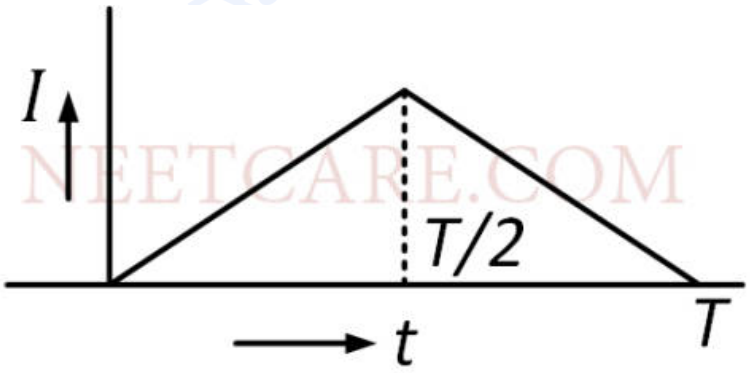Q45. AIPMT 2012 Prelims


Open solution

The current (I) in the inductance is varying with time according to the plot shown in figure.




Which one of the following is the correct variation of voltage with time in the coil ?


(A)

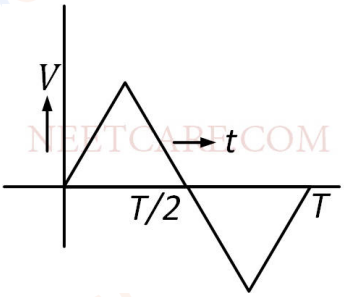

(B)

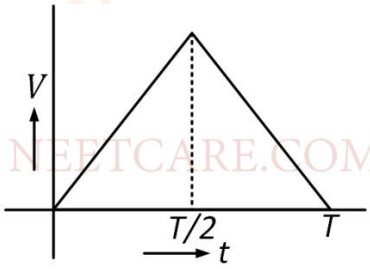


(C)

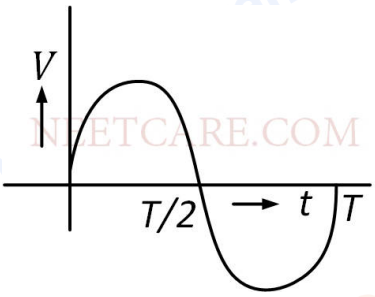

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play


(D)

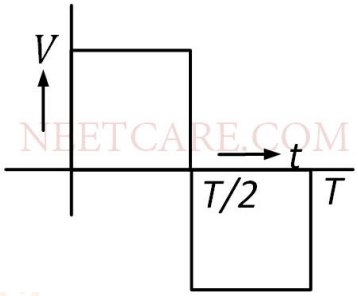

Q46. AIPMT 2011 Mains

The r.m.s. value of potential difference V shown in the figure is

Open solution

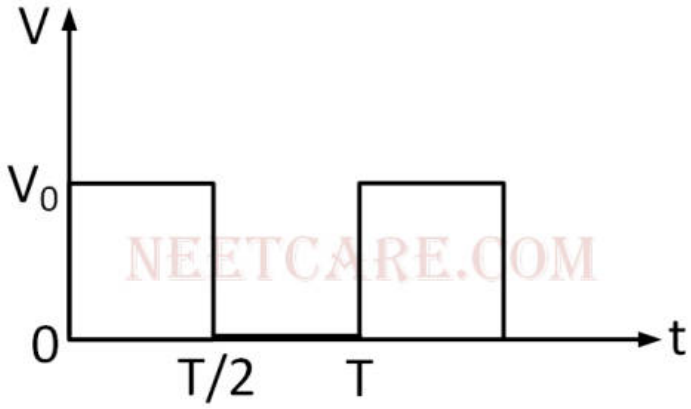

(A) $\frac{V_0}{\sqrt{3}}$ (B) V_0 (C) $\frac{V_0}{\sqrt{2}}$ (D) $\frac{V_0}{2}$

Q47. AIPMT 2011 Mains

A coil has resistance 30 ohm and inductive reactance 20 ohm at 50 Hz frequency. If an ac source, of 200 volt, 100 Hz, is connected across the coil, the current in the coil will be

Open solution

(A) 2.0 A (B) 4.0 A (C) 8.0 A (D) $\frac{20}{\sqrt{13}}A$

Q48. AIPMT 2011 Prelims

An ac voltage is applied to a resistance R and an inductor L in series. If R and the inductive reactance are both equal to 3 Ω, the phase difference between the applied voltage and the current in the circuit is

Open solution

(A) $\pi/6$ (B) $\pi/4$ (C) $\pi/2$ (D) zero

Q49. AIPMT 2011 Prelims

In the ac circuit an alternating voltage e = $200\sqrt{2}$sin100t volts is connected to a capacitor of capacity 1 μF. The r.m.s. value of the current in the circuit is

Open solution

(A) 10 mA (B) 100 mA (C) 200 mA (D) 20 mA

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q50. AIPMT 2010 Mains

A condenser of capacity C is charged to a potential difference of V_1. The plates of th condenser are then connected to an ideal inductor of inductance L. The current through the inductor when the potential difference across the condenser reduces to V_2 is

Open solution

(A) $\left(\frac{C(V_1-V_2)^2}{L}\right)^{\frac{1}{2}}$

(B) $\frac{C(V_1^2-V_2^2)}{L}$


(C) $\frac{C(V_1^2+V_2^2)}{L}$

(D) $\left(\frac{C(V_1^2-V_2^2)}{L}\right)^{\frac{1}{2}}$

Q51. AIPMT 2010 Prelims

In the given circuit the reading of voltmeter V_1 and V_2 are 300 volts each. The reading of the voltmeter V_3 and ammeter A are respectively

Open solution

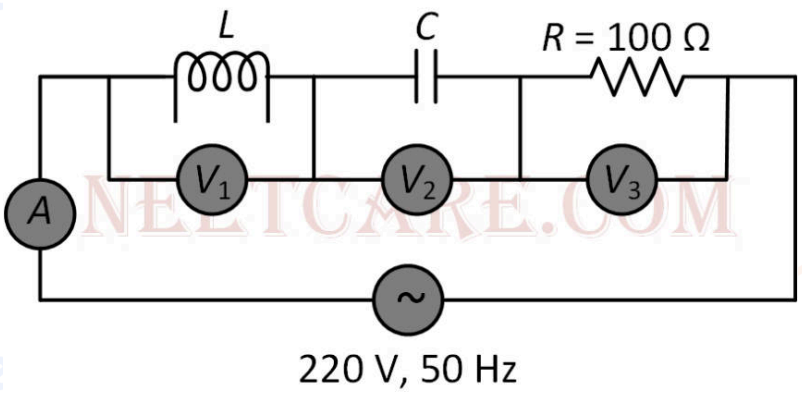

(A) 150V, 2.2A (B) 220V, 2.2A (C) 220V, 2.0A (D) 100V, 2.0A

Q52. AIPMT 2010 Prelims

A 220 volt input is supplied to a transformer. The output circuit draws a current of 2.0 ampere at 440 volts. If the efficiency of the transformer is 80%, the current drwn by the primary windings of the transformer is

Open solution

(A) 3.6 ampere (B) 2.8 ampere (C) 2.5 ampere (D) 5.0 ampere

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q53. AIPMT 2009

Power dissipated in an LCR series circuit connected to an A.C. source of emf ε is

(A) $\frac{\varepsilon^2\left[R^2+\left(L\omega-\frac{1}{C\omega}\right)^2\right]}{R}$

(B) $\frac{\varepsilon^2\sqrt{R^2+\left(L\omega-\frac{1}{C\omega}\right)^2}}{R}$

(C) $\frac{\varepsilon^2 R}{\sqrt{R^2+\left(L\omega-\frac{1}{C\omega}\right)^2}}$

(D) $\frac{\varepsilon^2 R}{\left[R^2+\left(L\omega-\frac{1}{C\omega}\right)^2\right]}$

Open solution

Q54. AIPMT 2008

In an a.c. circuit the e.m.f. (ε) and the current

(i) at any instant are given respectively by
$\varepsilon = E_0\sin\omega t$, $i = I_0\sin(\omega t - \phi)$

The average power in the circuit over one cycle of a.c. is

(A) $\frac{E_0 I_0}{2}\cos\phi$ (B) $E_0 I_0$ (C) $\frac{E_0 I_0}{2}$ (D) $\frac{E_0 I_0}{2}\sin\phi$

Open solution

Q55. AIPMT 2007

The primary and secondary coils of a transformer have 50 and 1500 turns respectively. If the magnetic flux ϕ linked with the primary coil is given by $\phi = \phi_0 + 4t$, where ϕ is webers, t is time in seconds and ϕ_0 is a constant, the output voltage across the secondary coil is

(A) 120 volt (B) 220 volts (C) 30 volts (D) 90 volts.

Open solution

Q56. AIPMT 2007

A transformer is used to light a 100 W and 110 V lamp from a 220 V mains. If the main current is 0.5 amp, the efficiency of the transformer is approximately

(A) 50% (B) 90% (C) 10% (D) 30%

Open solution

Q57. AIPMT 2007

What is the value of inductance L for which the current is maximum in a series LCR circuit with C = 10 μF and ω = 1000 s^{-1} ?

(A) 1 mH (B) cannot be calculated unless R is known
(C) 10 mH (D) 100 mH

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q58. AIPMT 2006

A coil of inductive reactance 31 Ω has a resistance of 8 Ω. It is placed in series with a condenser of capacitative reactance 25 Ω. The combination is connected to an a.c. source of 110 V. The power factor of the circuit is

Open solution

(A) 0.33 (B) 0.56 (C) 0.64 (D) 0.80

Q59. AIPMT 2006

The core of a transformer is laminated because

Open solution

(A) ratio of voltage in primary and secondary may be increased

(B) energy losses due to eddy currents may be minimised

(C) the weight of the transformer may be reduced

(D) rusting of the core may be prevented.

Q60. AIPMT 2006

A transistor-oscillator using a resonant circuit with an inductor L (of negligible resistance) and a capacitor C in series produce oscillations of frequency f. If L is doubled and C is changed to 4C, the frequency will be

Open solution

(A) $f/2$ (B) $f/4$ (C) $8f$ (D) $f/2\sqrt{2}$

Q61. AIPMT 2005

In a circuit L, C and R are connected in series with an alternating voltage source of frquency f. The current leads the voltage by 45°. The value of C is

Open solution

(A) $\frac{1}{\pi f(2\pi f\, L-R)}$ (B) $\frac{1}{2\pi f(2\pi f\, L-R)}$

(C) $\frac{1}{\pi f(2\pi f\, L+R)}$ (D) $\frac{1}{2\pi f(2\pi f\, L+R)}$

Q62. AIPMT 2004

A coil of 40 henry inductance is connected in series with a resistance of 8 ohm and the combination is joined to the terminals of a 2 volt battery. The time constant of the circuit is

Open solution

(A) 5 seconds (B) 1/5 seconds (C) 40 seconds (D) 20 seconds

Q63. AIPMT 2002

For a series LCR circuit the power loss at resonance is

Open solution

(A) $\frac{V^2}{\left[\omega L-\frac{1}{\omega C}\right]}$ (B) $I^2L\omega$

(C) I^2R (D) $\frac{V^2}{C\omega}$

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q64. AIPMT 2001

A capacitor of capacity C has reactance X. If capacitance and frequency become double then reactance will be

(A) 4X (B) X/2 (C) X/4 (D) 2X

Open solution

MCQ (More than One Correct Answer) 1 questions

Q65. AIPMT 2001

The value of quality factor is

(A) $\frac{\omega R}{L}$ (B) $\frac{1}{\omega RC}$ (C) $\sqrt{LC}$ (D) L/R

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Answer Key

MCQ (Single Correct Answer)

1. **B**	2. **D**	3. **D**	4. **D**	5. **D**
6. **A**	7. **B**	8. **B**	9. **B**	10. **D**
11. **A**	12. **A**	13. **D**	14. **C**	15. **D**
16. **B**	17. **C**	18. **B**	19. **D**	20. **D**
21. **B**	22. **C**	23. **B**	24. **A**	25. **B**
26. **B**	27. **D**	28. **B**	29. **B**	30. **D**
31. **A**	32. **B**	33. **C**	34. **C**	35. **A**
36. **C**	37. **D**	38. **D**	39. **C**	40. **B**
41. **C**	42. **B**	43. **D**	44. **C**	45. **D**
46. **C**	47. **B**	48. **B**	49. **D**	50. **D**
51. **B**	52. **D**	53. **D**	54. **A**	55. **A**
56. **B**	57. **D**	58. **D**	59. **B**	60. **D**
61. **D**	62. **A**	63. **C**	64. **C**	

MCQ (More than One Correct Answer)

65. **B**

For numerical answers given as a range, any value within the range is correct. Full solutions: scan the QR code next to each question, or visit questions.examside.com.

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

ExamGOAL
PYQ PDF

Your Exam. Our Responsibility.

From first chapter to exam day.

Practise with the questions your exam has already asked, then test yourself under real exam conditions.

PAST YEAR QUESTIONS

Every past paper, chapter-wise.

Previous year questions sorted the way you study, each with a full solution.

- Chapter-wise and year-wise
- Weightage and topic tags on every chapter
- Your progress on each one, at a glance

MOCK TESTS

Mock tests with a real exam feel.

Practise under the same pressure as the real paper, on your phone or on the big screen.

- Timed sections, just like exam day
- Mark questions for review and come back

ANALYSIS

Know your score. Know your rank.

A full report after every test, so you know exactly where you stand.

- Your percentile among everyone who took it
- Predicted real-exam percentile and All India Rank
- Subject breakdown and time analysis

PRACTICE

Solve. Check. Understand.

Learn from every question, not just the ones you get right.

- Instant answers as you practise
- Step-by-step explanations
- See how everyone else answered

NCERT Exemplar
With full solutions

Exam syllabus
Subject and chapter-wise

Bookmarks
Organised in groups

Your notes
On any question

ExamGOAL
LEARNING APP

ExamGOAL: Exam Preparation App

One app for every exam. Free trial for new users, on Android and the web.

GET IT ON Google Play

Scan to get the app

www.examgoal.com
Practice and mock tests

questions.examside.com
Free solutions

pdf.questions.examgoal.com
Free PYQ PDFs